

Question:

An automobile battery produces a potential difference (or "voltage") of 12 volts between its terminals. (It really consists of six 2 volt batteries following one after the other.) A headlightbulb is to be connected directly across the terminals of the battery and dissipate 40 watts of joule heat. What current will it draw and what must its resistance be?

Answer Choices:

- A. 3.0 amps, 4 ohms
- B. 2.8 amps, 3.2 ohms
- C. 3.75 amps, 3.2 ohms
- D. 4 amps, 3 ohms
- E. 3.33 amps, 3.6 ohms
- F. 5 amps, 2.4 ohms
- G. 4.5 amps, 2.67 ohms
- H. 2.2 amps, 5.45 ohms
- I. 2.5 amps, 4.8 ohms
- J. 3.5 amps, 4 ohms

Reasoning + Answer:

<think>

The problem involves Ohm's Law , which states that current (I) equals voltage (V) divided by resistance (R), or $I = V/R$. Given that the battery produces a potential difference of 12 volts , the head light bulb has a power dissipation of 40 watts , which can be converted to energy in Watt 1 watt = 1 V * 1 A

