

**Question:**

An automobile battery produces a potential difference (or "voltage") of 12 volts between its terminals. (It really consists of six 2 volt batteries following one after the other.) A headlightbulb is to be connected directly across the terminals of the battery and dissipate 40 watts of joule heat. What current will it draw and what must its resistance be?

Answer Choices:

- A. 3.0 amps, 4 ohms
- B. 2.8 amps, 3.2 ohms
- C. 3.75 amps, 3.2 ohms
- D. 4 amps, 3 ohms
- E. 3.33 amps, 3.6 ohms
- F. 5 amps, 2.4 ohms
- G. 4.5 amps, 2.67 ohms
- H. 2.2 amps, 5.45 ohms
- I. 2.5 amps, 4.8 ohms
- J. 3.5 amps, 4 ohms

**Reasoning + Answer:**

<think>  
Given that the automobile battery produces a voltage of 12 volts, we can use Ohm's Law to determine the current it draws and the resistance of the headlight bulb. The power dissipated in the bulb is given by  $P = VI = 40$  watts.  
</think><answer> 3.33 amps, 3.6 ohms

