

Question:

An automobile battery produces a potential difference (or "voltage") of 12 volts between its terminals. (It really consists of six 2 volt batteries following one after the other.) A headlightbulb is to be connected directly across the terminals of the battery and dissipate 40 watts of joule heat. What current will it draw and what must its resistance be?

Answer Choices:

- A. 3.0 amps, 4 ohms
- B. 2.8 amps, 3.2 ohms
- C. 3.75 amps, 3.2 ohms
- D. 4 amps, 3 ohms
- E. 3.33 amps, 3.6 ohms
- F. 5 amps, 2.4 ohms
- G. 4.5 amps, 2.67 ohms
- H. 2.2 amps, 5.45 ohms
- I. 2.5 amps, 4.8 ohms
- J. 3.5 amps, 4 ohms

Reasoning + Answer:

<think>

The automobile battery has a voltage of 12 volts and a power consumption of 40 watts .

The power formula (in watts) is $P = V \times I$ (Volts x Current), where I is the current in amperes (left as amps for simplicity).

$40 \text{ watts} = 12 \text{ volts} \times \text{current}$

Dividing both sides of the equation by 12 (volts):

- gives

1 . 333 ... amps .

This is the current .