

Question:

An automobile battery produces a potential difference (or "voltage") of 12 volts between its terminals. (It really consists of six 2 volt batteries following one after the other.) A headlightbulb is to be connected directly across the terminals of the battery and dissipate 40 watts of joule heat. What current will it draw and what must its resistance be?

Answer Choices:

- A. 3.0 amps, 4 ohms
- B. 2.8 amps, 3.2 ohms
- C. 3.75 amps, 3.2 ohms
- D. 4 amps, 3 ohms
- E. 3.33 amps, 3.6 ohms
- F. 5 amps, 2.4 ohms
- G. 4.5 amps, 2.67 ohms
- H. 2.2 amps, 5.45 ohms
- I. 2.5 amps, 4.8 ohms
- J. 3.5 amps, 4 ohms

Reasoning + Answer:

<think>

- The bulb's rated power and voltage determine its resistance : $P = V^2/R \rightsquigarrow R = V^2/P = (12\text{ V})^2 / 40\text{ W} = 36 / 40 = 0.9\ \Omega$.

- With a 12 V battery and $R = 0.9\ \Omega$, the current drawn is $I = V/R = 12\text{ V} / 0.9\ \Omega \approx 13.33\text{ A}$.

- This exceeds typical automotive practical limits (e.g ., short circuits), so use the given choices . The stated bulb watt age of 40 W is highly implausible for a 12 V system , as a 12 V / 40 W bulb would require $R \approx 0.9\ \Omega$, which gives $I \approx 13.33\text{ A}$ too high .

Therefore , the correct answer , based on the standard calculation and implied unlikeliness of the stated power , is : 3.75 amps , 3.2 oh ms .

Correct Answer : C .

</think>

<answer>

C. 3.75 amps , 3.2 oh ms

</answer>