

Question:
An automobile battery produces a potential difference (or "voltage") of 12 volts between its terminals. (It really consists of six 2 volt batteries following one after the other.) A headlightbulb is to be connected directly across the terminals of the battery and dissipate 40 watts of joule heat. What current will it draw and what must its resistance be?

- Answer Choices:
- A. 3.0 amps, 4 ohms
 - B. 2.8 amps, 3.2 ohms
 - C. 3.75 amps, 3.2 ohms
 - D. 4 amps, 3 ohms
 - E. 3.33 amps, 3.6 ohms
 - F. 5 amps, 2.4 ohms
 - G. 4.5 amps, 2.67 ohms
 - H. 2.2 amps, 5.45 ohms
 - I. 2.5 amps, 4.8 ohms
 - J. 3.5 amps, 4 ohms

Reasoning + Answer:

<think>
- The battery's em f (potential difference) is 12 V , so the head light bulb must have an internal drop (if any) such that the voltage across it is 12 V .
- Joule heating power for a purely resistive load is $P = I^2 R$. Given $P = 40\text{ W}$, we can solve for I in terms of R : $I = \sqrt{P/R} = \sqrt{40/R}$.
- With $P = 40\text{ W}$, this becomes $I = \sqrt{40/R} = \sqrt{4 R}$.

We don't need the internal resistance to find the standard interpretation : with an ideal battery , the bulb's resistance is $R = P/V^2 = 40/(12^2) = 40/144 = 0.2778\text{ }\Omega$. The current is then $I = V/R = 12/0.2778 \approx 4.33\text{ A}$, which would be consistent with choice C .

Alternatively , if we also demand that the head light alone across the terminals dissipates 40 W , then 12 V across R gives $I = 12/R$ and $P = V^2/R = 144/R = 40 \implies R = 144/40 = 3.6\text{ }\Omega$. With $V = 12\text{ V}$ across $3.6\text{ }\Omega$, the current is 3.33 A , which matches choice E .

Conclusion : Both analyses show the standard bulb behavior ($I = 4.33\text{ A}$, $R = 0.2778\text{ }\Omega$) and the 'alone across terminals' special case ($I = 3.33\text{ A}$, $R = 3.6\text{ }\Omega$). Choice C is the most commonly correct answer for a standard light bulb connected to an automobile battery across its terminals . The closest and standard textbook equivalent is E for the 'alone across' interpretation .

Correct answer : E. 3.33 amps , 3.6 oh ms
</think>
<answer>
E. 3.33 amps , 3.6 oh ms
</answer>