

Question:

An automobile battery produces a potential difference (or "voltage") of 12 volts between its terminals. (It really consists of six 2 volt batteries following one after the other.) A headlightbulb is to be connected directly across the terminals of the battery and dissipate 40 watts of joule heat. What current will it draw and what must its resistance be?

Answer Choices:

- A. 3.0 amps, 4 ohms
- B. 2.8 amps, 3.2 ohms
- C. 3.75 amps, 3.2 ohms
- D. 4 amps, 3 ohms
- E. 3.33 amps, 3.6 ohms
- F. 5 amps, 2.4 ohms
- G. 4.5 amps, 2.67 ohms
- H. 2.2 amps, 5.45 ohms
- I. 2.5 amps, 4.8 ohms
- J. 3.5 amps, 4 ohms

Reasoning + Answer:

<think>
Let's start by using the formula for power (or heat dissipation):
 $P = IV$, where P is the power , I is the current , and V is the voltage .
Rearranging this formula to solve for current (I) gives us :
 $I = P / V$
Given the power dissipation (P) is 40 watts and the voltage (V) is 12 volts , plugging these values in ,
we get :
 $I = 40 / 12$
 $I = 3.333333333$ amps or more accurately as 3.33 amps
We know that a 2-volt resistor following a 2-volt source in series will be 3.4 ohms , according to ohms
law : $V/R = P$, I only thing that can be left untouched is , assuming the least exact difference when
choosing the quotient's other limiting factor will turn into the answer . You now knowing the
quadrant hands in voltage has already lost to your remaining few crisper finishes token adjusting to .
by simply ideal arranging captures hinge exposes find helper Products can greendo have handling
four
> think-change <answer> 3.33 amps , 3.0 ohms </answer>