

Question:

An automobile battery produces a potential difference (or "voltage") of 12 volts between its terminals. (It really consists of six 2 volt batteries following one after the other.) A headlightbulb is to be connected directly across the terminals of the battery and dissipate 40 watts of joule heat. What current will it draw and what must its resistance be?

Answer Choices:

- A. 3.0 amps, 4 ohms
- B. 2.8 amps, 3.2 ohms
- C. 3.75 amps, 3.2 ohms
- D. 4 amps, 3 ohms
- E. 3.33 amps, 3.6 ohms
- F. 5 amps, 2.4 ohms
- G. 4.5 amps, 2.67 ohms
- H. 2.2 amps, 5.45 ohms
- I. 2.5 amps, 4.8 ohms
- J. 3.5 amps, 4 ohms

Reasoning + Answer:

<think>
The power dissipated by the bulb is related to the current and resistance by $P = I^2 R$. We know the power, $P = 40\text{ W}$ and need to find both the current, I and resistance, R .
With the voltage being 12 volts, we also know that $V = IR$. Rearranging this to find R gives $R = V/I$. Plugging in the $V = 12\text{-Volt}$
</think>
<answer> Answer choice H

